



65122

I Semester B.C.A. Degree Examination, March/April 2022
(CBCS Scheme)
COMPUTER SCIENCE
Digital Electronics

Time : 3 Hours

Max. Marks : 70

Instruction : Answer **all** Sections.

SECTION – A

I. Answer **any ten** questions.

(10×2=20)

- 1) State Ohms Law.
- 2) Give the equivalent resistance for two resistors in series and parallel.
- 3) Define Kirchhoff's current Law.
- 4) Define frequency and cycle with respect to AC waveform.
- 5) What is Conductor and Insulators ?
- 6) What is Intrinsic and Extrinsic semiconductors ?
- 7) What is Doping ?
- 8) Find the 2's complement of 0011001.
- 9) Prove that $A + AB = A$.
- 10) Write the logical symbol and truth table of NOR gate.
- 11) What is combinational circuit ?
- 12) What is ASCII ?



SECTION – B

II. Answer **any five** questions.

(5×10=50)

- 13) a) State and explain Norton's theorem. 5
- b) State and explain superposition theorem. 5

P.T.O.