



- 14) a) Convert $(9AB)_{16}$ to $()_2$, $()_8$, $()_{10}$. 5
 b) Subtract $(29)_{10} - (7)_{10}$ using 2's complement. 5
- 15) a) State and prove Demorgan's Law. 5
 b) Simplify using K-Map
 $F = \sum m (1, 5, 7, 8, 9, 13) + \sum d (3, 12)$. 5
- 16) a) What is rectifier ? Explain half-wave rectifier. 5
 b) Differentiate encoder and decoder. 5
- 17) a) Realize the basic gates using NAND Gate. 5
 b) Explain Half adder with truth table and logic circuit. 5
- 18) a) What is multiplexer ? Explain 4-to-1 multiplexer. 5
 b) Explain the working of SR flip flop. 5
- 19) a) Explain different energy Bands. 5
 b) Differentiate forward biasing and reverse biasing. 5
- 20) a) Explain SISO and PIPO shift register. 5
 b) Write a brief note on applications of shift register. 5

SECTION - B

(2x10=20)

2

5

P.T.O.